

Class 10 Physics - Ohm's Law

Board: CBSE

Topic: Current and Resistance

Question: Calculate current if $V = 12V$ and $R = 4 \text{ ohm}$.

Formula: $V = I R$

Draw circuit diagram and explain each component.