

Class 10 Physics

Topic: Ohm's Law

Q. Calculate current if $V = 12V$ and $R = 4 \text{ ohm}$.